

# FAST AMPLITUDE STABILIZATION OF AN RC OSCILLATOR

*This technique for stabilizing the output amplitude of an RC sine-wave oscillator uses a multiphase rectifier to convert the oscillator output to d.c. This voltage does not require further filtering, which results in a short amplitude settling time. An experimental circuit demonstrates the technique.*

by I. M. Filanovskiy  
V. A. Piskarev  
and K. A. Stromsmoe\*

A stable sine-wave oscillator with amplitude control usually incorporates a voltage-controlled attenuator. The d.c. input to this attenuator must have a very small ripple to avoid excessive distortion of the output waveform. If this direct voltage is derived from the usual half-wave rectifier, an extremely large filter time constant is required: the oscillator output level consequently settles very slowly. This behaviour is undesirable in low-frequency applications. Several solutions have been proposed to solve these problems, one of which has been to combine analogue and digital circuitry to use amplitude sampling<sup>1,2</sup> or correction to the capacitor initial conditions,<sup>3,4</sup>. This involves relatively complicated circuits. A more direct and simpler circuit approach is to use oscillator networks with available four-phase voltage<sup>5</sup> or multiphase oscillators<sup>6</sup> with the rectified, multiphased voltage obtained from the oscillator. The circuit proposed here also uses multiphase rectified voltages, but these voltages are obtained in a special circuit from two sinusoidal voltages shifted by 90°. The circuit consists of summing operational amplifiers.

The full circuit of the RC oscillator with the eight-phase rectifier is shown in Fig. 1. It includes an RC resonator (operational amplifiers A<sub>1</sub>, A<sub>2</sub> and A<sub>3</sub>) with the voltage-controlled attenuator (the transconductance amplifier g<sub>m</sub> and resistors R<sub>7</sub> to R<sub>8</sub>); the control circuit with the error amplifier A<sub>4</sub> and the two-stage multiphase rectifier (the operational amplifiers A<sub>5</sub> to A<sub>10</sub> and diodes D<sub>1</sub>–D<sub>8</sub>) mentioned above.

Two sinusoidal voltages V<sub>1</sub> and V<sub>7</sub> of equal amplitudes are applied to the inputs of two inverting operational amplifiers A<sub>5</sub> and A<sub>6</sub> in the first stage. At the output of this first stage we obtain four sinusoidal voltages shifted with respect to each other by 90° (Fig. 2(a)). The second stage produces eight sinusoidal voltages shifted with respect to each other by 45° (Fig. 2(b)). Here we use the fact that operational amplifier produces vector summation of the voltages applied to its inverting input. For example

$$\dot{V}_6 = -\frac{1}{\sqrt{2}}\dot{V}_1 - \frac{1}{\sqrt{2}}\dot{V}_3 \quad (1)$$

where  $\dot{V}_1$ ,  $\dot{V}_3$  and  $\dot{V}_6$  are phasors corresponding to v<sub>1</sub>, v<sub>3</sub> and v<sub>6</sub>.

The multiplying factor 1/√2 in (1) is achieved by the special choice of the resistors connected to the operational amplifier A<sub>10</sub>. Changing their values we could obtain a phase shift of V<sub>6</sub> with respect to V<sub>1</sub> and V<sub>3</sub> which is different from ±135°. Thus, in principle, we can obtain any m-phase voltage system if we have two sinusoidal voltages with phase shift different from 0° and 180°. The output voltages appear simultaneously with the input voltages and the multiphase rectifier produces the output d.c. voltage.

$$V_R = \frac{\sin \pi/m}{\pi/m} V_m$$

where V<sub>m</sub> is the amplitude of the m-phase voltage. The multiplier  $\sin \pi/m \div \pi/m$  approaches unity when m increases (for m=8 it is equal to 0.975). Hence, such an m-phase rectifier can be used as a unit which produces a direct voltage proportional to the oscillation amplitude and without any delay (theoretically, at least), with low harmonic content. The requirement of any additional filtering when m increases is eliminated.

The output voltage of the operational amplifier A<sub>1</sub> coincides in phase with V<sub>5</sub>. We could use it and save one operational amplifier in the first stage. But the voltages V<sub>1</sub> and V<sub>7</sub> have the lowest amount of harmonics and using only these two voltages we obtain less total harmonic distortion (t.h.d.) at the oscillator output.

In the steady-state condition, the output voltage amplitude of the oscillator is determined by the equality

$$V_R = E_R$$

where E<sub>R</sub> is the reference voltage. The amplitude control system is a Type 1 system due to the fact that an RC oscillator

acts as an integrator with respect to an amplitude change<sup>1,7</sup> in the amplitude control system.

During the static oscillations the condition

$$g_m \frac{R_7}{R_6 + R_7} = \frac{1}{R_5}$$

is satisfied.

The transconductance g<sub>m</sub> is determined by the d.c. control current I<sub>c</sub> in the resistor R<sub>8</sub> and, for the CA 3080 transconductance amplifier which we used in our experiments,

$$g_m \approx \frac{I_c}{2V_T}$$

where V<sub>T</sub> is threshold voltage<sup>8</sup> (V<sub>T</sub> ≈ 26mV at 300°K). The resistors R<sub>6</sub> and R<sub>7</sub> are chosen from the condition that

$$V_7 \cdot \frac{R_7}{R_6 + R_7} \leq V_T$$

where V<sub>7</sub> is the amplitude of v<sub>7</sub>. This ensures the linear operation of the transconductance amplifier. The value of R<sub>8</sub> was chosen in such a way that the control current I<sub>c</sub> (in the steady state condition) is approximately equal to one half of the maximum control current allowable for linear operation. The control input (pin 5) d.c. potential is close to the negative of the power supply for CA 3080. In this case, the linear operation will be preserved for the whole output voltage range of the error amplifier A<sub>4</sub> and at the same time the value of R<sub>5</sub> will be low. As a result the displacement of poles from the jω-axis into the left

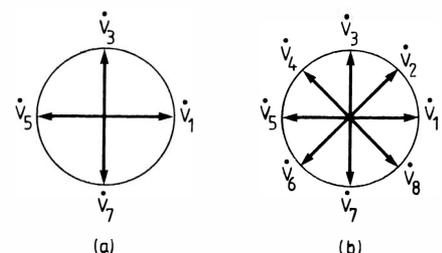


Fig. 2. Output voltages in multiphase rectifier (a) first stage (b) second stage

\* University of Alberta, Edmonton, Alberta.

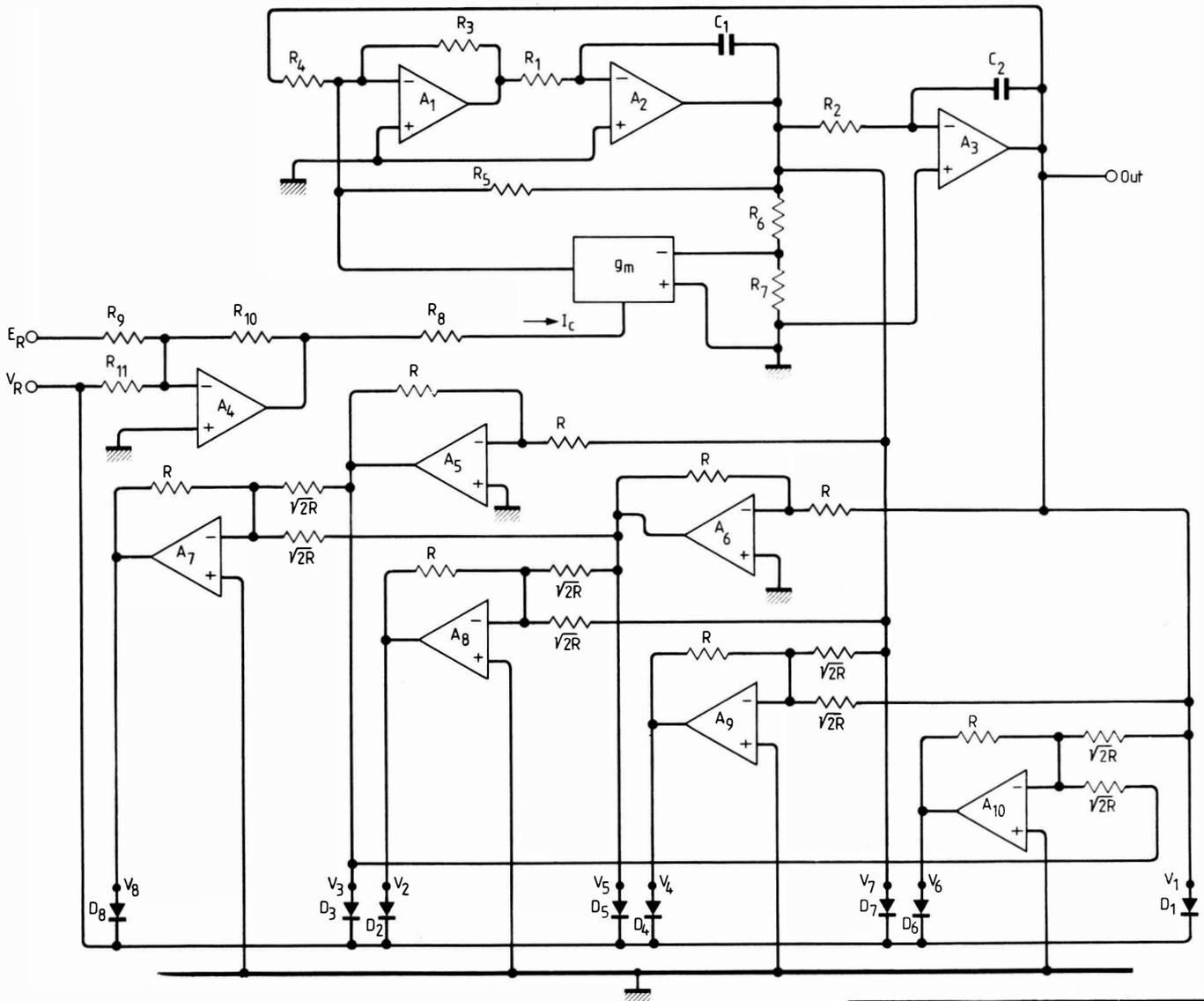


Fig. 1. RC oscillator with multiphase rectifier

or right half plane due to the sudden change in the  $E_R$  level will be maximum and the transient response duration will be shortened.

The output voltage of the multiphase rectifier includes the small ripple voltage also. The amplitude of the  $k$ -th harmonic equals

$$a_k = 2V_m \cdot \frac{\sin \pi/m}{\pi/m} \cdot \frac{(-1)^{k+l}}{k^2 m^2 - 1}$$

This ripple voltage will be amplified in  $A_4$  and applied to the control input modulating the transconductance  $g_m$ . The approach used by Vannerson and Smith<sup>5</sup> allows us to calculate the output distortion voltage which consists of only two significant harmonics given by

$$v_d = \frac{1}{2} \frac{R_3}{R_8} \cdot \frac{R_{10}}{R_{11}} \cdot \frac{V_m^2}{V_T} \frac{R_7}{(R_7 + R_6)} \cdot \frac{\sin \pi/m}{\pi/m}$$

$$\left[ \frac{1}{(m^2 - 1)} \left( \frac{\cos(m-1)\omega_0}{(m-1)^2 - 1} + \frac{\cos(m+1)\omega_0}{(m+1)^2 - 1} \right) \right]$$

where  $\omega_0$  is the oscillator frequency.

In the test oscillator,

- $R_1, R_2, R_3, R_4$  15k $\Omega$
- $R_5$  47k $\Omega$ ,  $R_6$  39k $\Omega$
- $R_7$  100 $\Omega$ ,  $R_8$  33k $\Omega$
- $R_9, R_{11}$  75k $\Omega$
- $R_{10}$  220k $\Omega$ ,  $R$  15k $\Omega$
- $C_1, C_2$ , 10nF.

For the output amplitude of  $V_1 = 10V$ , the total harmonic distortion is 0.2% approximately. Further reduction of the t.h.d. can be obtained by reducing the ratio  $R_{10}/R_{11}$ .

Figure 3 shows the transient response of this oscillator when the reference voltage  $E_R$  is modulated by a 60Hz square wave that changes from 10 to 6.6V. The transient response duration is not more than two periods of the output voltage.

If the ratio  $R_{10}/R_{11}$  is decreased to 1 (decreasing the t.h.d. to less than 0.01%) the transient response duration will increase from 2 to 5 periods which is also acceptable in many cases.

The control zone is from 0.7V (or 0.3V if we use germanium diodes) to saturation voltage of operational amplifiers.

### References

1. D. Meyer-Ebrecht. Schnelle Amplitudenregelung harmonischer Oszillatoren. Phillips Res. Repts. Suppl. 1974 No. 6.
2. E. Vannerson, K. C. Smith. A low distortion oscillator with fast amplitude stabilization. *Int. J. Electronics*, vol. 39, No. 4., pp. 465-472, 1975.
3. N. Vannai, L. Pap. RC-oscillator with extremely low harmonic distortion period. *Polytech. Electr. Engrg* (Hungary), vol. 24 No. 1-2, pp. 59-65, 1980.

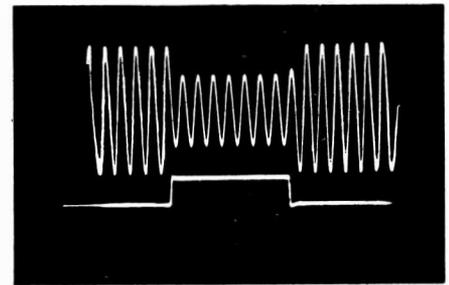


Fig. 3. Modulation of the reference voltage and the oscillator output voltage.

4. J. Pahor, J. Fettich, M. Tavzes. A harmonic oscillator with low harmonic distortion and stable amplitude. *Int. J. Electronics*, vol. 37, No. 6, pp. 765-768, 1974.

5. E. Vannerson, K. C. Smith. Fast amplitude stabilization of an RC-oscillator. *IEEE Journal of Solid-state circuits*, vol. SC-9 No. 4, pp. 176-179, 1974.

6. A. D. Ryder. Multiphase low-distortion oscillator. *Wireless World*, vol. 87, No. 1540, pp. 59-60, 1981.

7. E. M. Kashoro, I. M. Filanovsky, K. A. Stromsmoe. A high frequency RC-oscillator with amplitude stabilization. Proc 24th Midwest Symp. on Circuits and Systems, Albuquerque, N. M. 1981 (to be published).

8. D. Gray, R. Meyer. Analysis and Design of Analog Integrated Circuits, J. Wiley, N. Y. 1977. www.keith-snook.info