



These tables give the relative values of R and C for 'lumped' networks capable of performing RIAA record replay equalisation where τ_3 is the 'break point' ($-3dB$) of the lowest frequency and τ_1 that of the highest. The results are based on calculations published in Wireless World 1957 by W. H. Livy of E.M.I Studios London (*now Abbey Road Studios*). In 1982 I expanded the calculations to include the 4th possible variant (*but not a 4th time constant*) and to show the numerical results of all the combinations of R and C. In 1985 the results were used to make a simple iterative program that enabled entry of any one component value to calculate the other three. The 'voltage driven' networks should be inserted between a low output impedance amplifier and a high input impedance amplifier to create a passive RIAA 'phono stage'. The 2 terminal variants are suitable for inclusion in negative feedback loops or can be 'current driven' with the output voltage developed across the network and amplified by a high input impedance amplifier. Keith Snook ~ www.keith-snook.info

It is obvious why this circuit with its nice symmetry became a favourite from the beginning for feedback record reply equalisers ~ RIAA or otherwise.

Rather than simplifying some formulae some were expanded to show repeating block patterns which later helped simplify my program.

$$\frac{R_1}{R_2} = \frac{\tau_1 + \tau_3 - \tau_2 - \frac{\tau_1 \cdot \tau_3}{\tau_2}}{\tau_2} = 6.877$$

$$\frac{R_3}{R_4} = \frac{\tau_1 + \tau_3 - \tau_2}{\tau_2 - \frac{\tau_1 \cdot \tau_3}{\tau_1 + \tau_3 - \tau_2}} = 12.4$$

$$\frac{R_5}{R_6} = \frac{\tau_3 - \tau_2}{\tau_2 - \tau_1} = 11.77$$

$$\frac{R_7}{R_8} = \frac{\tau_1 + \tau_3 - \tau_2 - \frac{\tau_1 \cdot \tau_3}{\tau_2}}{\tau_2} = 6.877$$

$$R_2 \cdot C_1 = \frac{\tau_1 \cdot \tau_3}{\tau_1 + \tau_3 - \tau_2 - \frac{\tau_1 \cdot \tau_3}{\tau_2}} = 109 \mu s$$

$$R_4 \cdot C_3 = \tau_2 - \frac{\tau_1 \cdot \tau_3}{\tau_1 + \tau_3 - \tau_2} = 236.8 \mu s$$

$$R_6 \cdot C_5 = \tau_3 \cdot \frac{\tau_2 - \tau_1}{\tau_3 - \tau_2} = 270 \mu s$$

$$R_8 \cdot C_7 = \tau_2 \cdot \frac{\tau_1 + \tau_3 - \frac{\tau_1 \cdot \tau_3}{\tau_2}}{\tau_1 + \tau_3 - \tau_2 - \frac{\tau_1 \cdot \tau_3}{\tau_2}} = 364.24 \mu s$$

$$R_2 \cdot C_2 = \tau_2 = 318 \mu s$$

$$R_4 \cdot C_4 = \frac{\tau_1 \cdot \tau_3}{\tau_1 + \tau_3 - \tau_2} = 81.2 \mu s$$

$$R_6 \cdot C_6 = \tau_1 = 75 \mu s$$

$$R_8 \cdot C_8 = \frac{\tau_1 \cdot \tau_3}{\tau_1 + \tau_3 - \frac{\tau_1 \cdot \tau_3}{\tau_2}} = 95.2 \mu s$$

$$R_1 \cdot C_1 = \frac{\tau_1 \cdot \tau_3}{\tau_2} = 750 \mu s$$

$$R_3 \cdot C_3 = \tau_1 + \tau_3 - \tau_2 = 2937 \mu s$$

$$R_5 \cdot C_5 = \tau_3 = 3180 \mu s$$

$$R_7 \cdot C_7 = \tau_1 + \tau_3 - \frac{\tau_1 \cdot \tau_3}{\tau_2} = 2505 \mu s$$

$$R_1 \cdot C_2 = \tau_1 + \tau_3 - \tau_2 - \frac{\tau_1 \cdot \tau_3}{\tau_2} = 2187 \mu s$$

$$R_3 \cdot C_4 = \frac{\tau_1 \cdot \tau_3}{\tau_2 - \frac{\tau_1 \cdot \tau_3}{\tau_1 + \tau_3 - \tau_2}} = 1007.2 \mu s$$

$$R_5 \cdot C_6 = \tau_1 \cdot \frac{\tau_3 - \tau_2}{\tau_2 - \tau_1} = 883.3 \mu s$$

$$R_7 \cdot C_8 = \frac{\tau_1 \cdot \tau_3}{\tau_2} \cdot \frac{\tau_1 + \tau_3 - \tau_2 - \frac{\tau_1 \cdot \tau_3}{\tau_2}}{\tau_1 + \tau_3 - \frac{\tau_1 \cdot \tau_3}{\tau_2}} = 654.79 \mu s$$